# PARAMETERIZED ALU
# DESIGN AND VERIFICATION REPORT

**Author Name:** AKILAN K

**Employee ID:** 6878

**Date:** May 11, 2026

# 1. PROJECT INTRODUCTION

This project presents the design and verification of a parameterized Arithmetic Logic Unit (ALU) capable of performing both arithmetic and logical operations on unsigned and signed operands. The ALU is designed with configurable data width, making it adaptable for various applications ranging from simple microcontrollers to complex digital signal processing systems.

**Purpose of the Design:** The ALU serves as the computational core of any processor, performing arithmetic operations (addition, subtraction, multiplication), logical operations (AND, OR, XOR, shift, rotate), and comparison operations.

**Main Functionality:**

- Arithmetic operations with configurable latency (1-cycle and 2-cycle)
- Logical and bitwise operations
- Signed and unsigned operation support
- Error detection for invalid operations
- Overflow and carry flag generation

**Verification Goals:**

- Achieve >90% code coverage using QuestaSIM
- Verify all 26 operation codes (13 arithmetic + 13 logical)
- Test all valid and invalid input combinations
- Validate corner cases including boundary conditions and overflow scenarios

# 2. OBJECTIVES

- Study the architecture of parameterized ALU designs and understand the trade-offs between area, speed, and functionality
- Implement synthesizable Verilog RTL code for a complete ALU with support for both arithmetic and logical operations
- Create comprehensive testbenches that verify all operations under various input conditions and corner cases
- Verify corner cases including boundary values, overflow conditions, invalid operations, and all valid/invalid input validity combinations
- Perform coverage analysis using industry-standard tools (QuestaSIM) to ensure verification completeness
- Document the complete verification process including test results, coverage metrics, and design observations

# 3. DESIGN ARCHITECTURE

## 3.1 Architecture Overview

The ALU follows a three-stage pipeline architecture to manage different operation latencies:

1. **Input Stage:** Captures and registers inputs when C_En is asserted
2. **Execution Stage:** Performs the requested operation (1 or 2 cycles depending on operation)
3. **Output Stage:** Updates output registers with results and status flags

## 3.2 Inputs

| Signal | Width | Description |
|---|---|---|

| | | |
|---|---|---|
| clk | 1 bit | System clock |
| rst | 1 bit | Asynchronous reset |
| M | 1 bit | Mode select (1 = Arithmetic, 0 = Logical) |
| C_En | 1 bit | Compute enable / Input capture enable |
| C_in | 1 bit | Carry input for arithmetic operations |
| Op_A | WIDTH bits | Operand A |
| Op_B | WIDTH bits | Operand B |
| In_V | 2 bits | Input validity indicator |
| Cmd | 4 bits | Operation command (0-13 for each mode) |

## 3.3 Outputs

| Signal | Width | Description |
|---|---|---|
| Res | 2Ã—WIDTH bits | Result of the operation |
| OFlow | 1 bit | Overflow flag for signed/unsigned operations |

| | | |
|---|---|---|
| C_out | 1 bit | Carry out for arithmetic operations |
| G | 1 bit | Greater than flag (A > B) |
| L | 1 bit | Less than flag (A < B) |
| E | 1 bit | Equal flag (A == B) |
| Err | 1 bit | Error flag for invalid operations |

## 3.4 Block Diagram

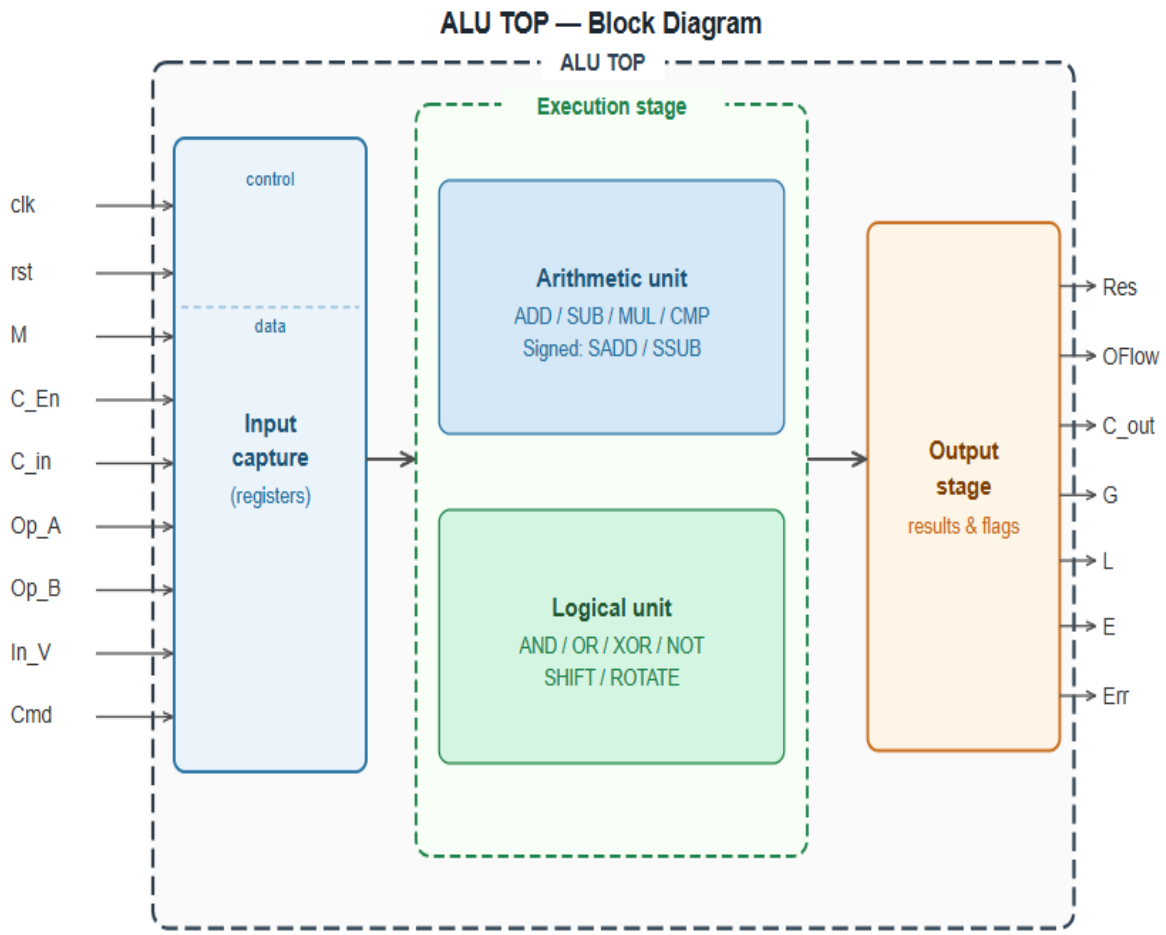

## 3.5 Timing Behaviour

- **1-cycle operations:** ADD, SUB, ADD with CIN, SUB with CIN, INC, DEC, CMP, all logical operations, signed ADD/SUB
- **2-cycle operations:** Multiplication operations (MUL1 and MUL2)

**Pipeline Flow:**

1. **Cycle 1 (C_En=1):** Inputs are captured into internal registers
2. **Cycle 2:** Execution begins (1-cycle operations complete)
3. **Cycle 3:** Results are available at outputs (for 1-cycle ops)
4. **For 2-cycle ops:** Additional cycle required for multiplication

# 4. SUPPORTED OPERATIONS

## 4.1 Arithmetic Operations (M=1)

| Cmd | Operation | Description | Latency | Valid In_V |
|---|---|---|---|---|
| 0 | ADD | A + B | 1 cycle | 2'b11 |
| 1 | SUB | A - B | 1 cycle | 2'b11 |
| 2 | ADD_CIN | A + B + C_in | 1 cycle | 2'b11 |
| 3 | SUB_CIN | A - B - C_in | 1 cycle | 2'b11 |
| 4 | INC_A | A + 1 | 1 cycle | 2'b11, 2'b01 |
| 5 | DEC_A | A - 1 | 1 cycle | 2'b11, 2'b01 |
| 6 | INC_B | B + 1 | 1 cycle | 2'b11, 2'b10 |

| | | | | |
|---|---|---|---|---|
| 7 | DEC_B | B - 1 | 1 cycle | 2'b11, 2'b10 |
| 8 | CMP | Compare A and B | 1 cycle | 2'b11 |
| 9 | MUL1 | (A+1) Ã— (B+1) | 2 cycles | 2'b11 |
| 10 | MUL2 | (A< | 2 cycles | 2'b11 |
| 11 | SADD | Signed A + B | 1 cycle | 2'b11 |
| 12 | SSUB | Signed A - B | 1 cycle | 2'b11 |

## 4.2 Logical Operations (M=0)

| Cmd | Operation | Description | Valid In_V |
|---|---|---|---|
| 0 | AND | A & B | 2'b11 |
| 1 | NAND | ~(A & B) | 2'b11 |
| 2 | OR | A \| B | 2'b11 |
| 3 | NOR | ~(A \| B) | 2'b11 |
| 4 | XOR | A ^ B | 2'b11 |

| | | | |
|---|---|---|---|
| 5 | XNOR | ~(A ^ B) | 2'b11 |
| 6 | NOT_A | ~A | 2'b11, 2'b01 |
| 7 | NOT_B | ~B | 2'b11, 2'b10 |
| 8 | SHR_A | A >> 1 | 2'b11, 2'b01 |
| 9 | SHL_A | A << 1 | 2'b11, 2'b01 |
| 10 | SHR_B | B >> 1 | 2'b11, 2'b10 |
| 11 | SHL_B | B << 1 | 2'b11, 2'b10 |
| 12 | ROL | Rotate Left A by B | 2'b11 |
| 13 | ROR | Rotate Right A by B | 2'b11 |

# 5. WORKING OF THE DESIGN

## Phase 1: Input Capture (First Pipeline Stage)

When C_En is asserted on a rising clock edge, inputs Op_A, Op_B, Cmd, and M are captured into internal registers (O_A, O_B, O_Cmd, O_M). These registered values are used for the execution phase.

## Phase 2: Operation Execution (Second Pipeline Stage)

The execution stage contains two parallel datapaths:

- **Arithmetic Datapath (M=1):** Performs ADD, SUB, multiplication, comparison, and signed operations
- **Logical Datapath (M=0):** Performs bitwise operations, shifts, and rotates

## Phase 3: Output Generation (Third Pipeline Stage)

On the next clock edge after execution completes, Res is updated with the computed Inter value and status flags (OFlow, C_out, G, L, E, Err) are updated.

# 6. TESTBENCH ARCHITECTURE

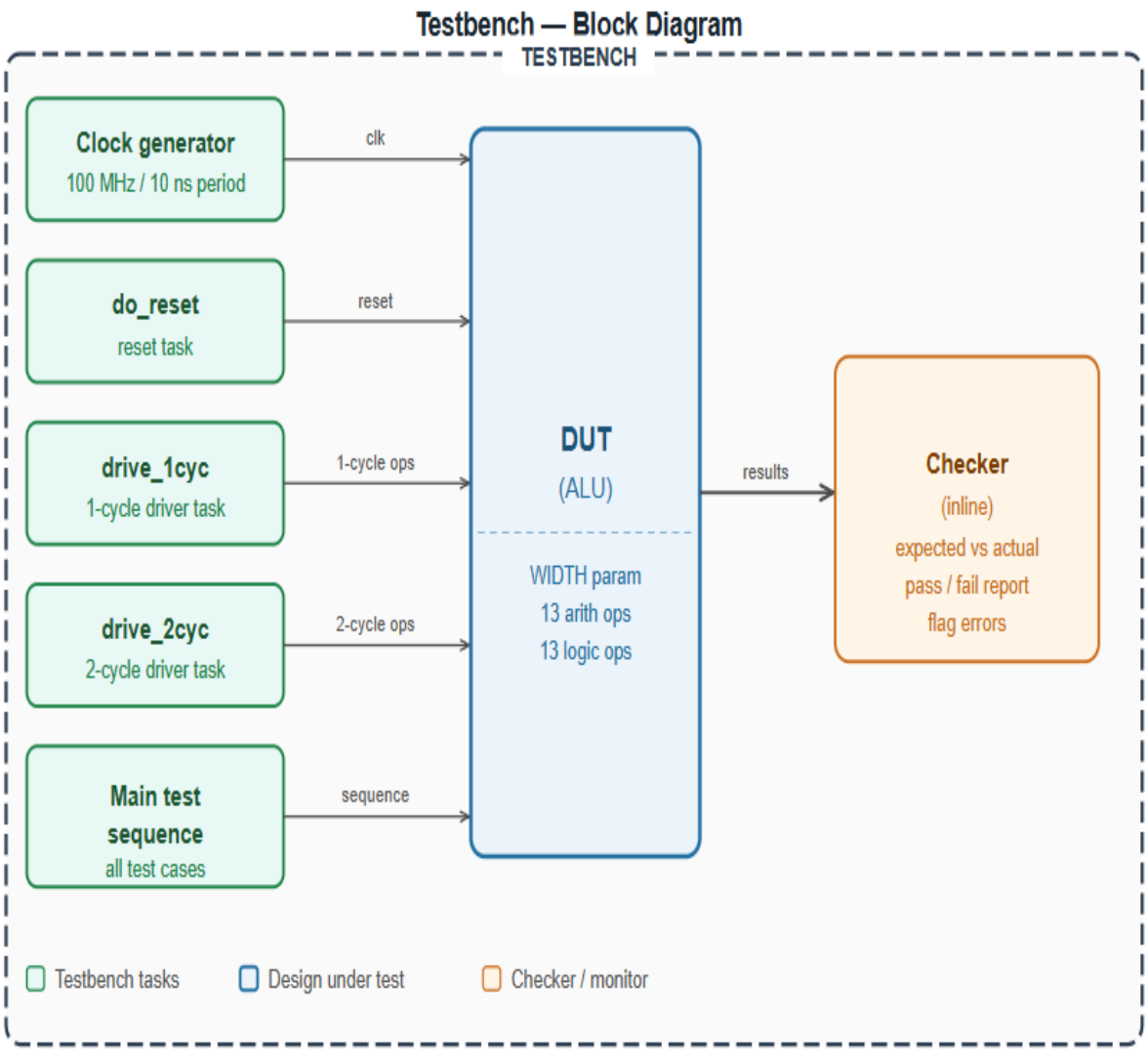

# 7. TESTBENCH COMPONENTS

## 7.1 Clock Generator

```
initial clk = 0;
always #5 clk = ~clk;
```

Generates a 100MHz clock (10ns period, 5ns half-cycle).

## 7.2 Reset Task (do_reset)

Performs a complete reset sequence: asserts reset for 3 clock cycles, deasserts all input signals, releases reset and waits for one cycle.

## 7.3 1-Cycle Driver Task (drive_1cyc)

Drives inputs for single-cycle operations and checks results after 3 clock cycles.

## 7.4 2-Cycle Driver Task (drive_2cyc)

Similar to drive_1cyc but waits 4 clock cycles to accommodate multi-cycle operations.

## 7.5 Main Test Sequence

Calls all test cases covering all arithmetic and logical operations with valid/invalid In_V combinations, edge cases, overflow scenarios, invalid commands, and mode transitions.

# 8. QUALITY OF CODE ASSESSMENT

## Lint Checks

- **No inferred latches:** All signals are properly initialized
- **No combinational loops:** All logic is synchronous
- **Proper reset conditions:** All registers have defined reset values
- **Signal width matching:** All assignments respect signal widths

## Code Review Findings

1. **Mixed Reset Polarity:** The design uses both posedge and negedge reset - intentional but requires careful handling.
2. **Multi-cycle Implementation:** Uses 'x' output on first cycle of multiplication - acceptable but simulation-only behavior.
3. **Signed Operations:** Proper use of $signed() system task for signed arithmetic.
4. **COUT generation is incorrect** for multiple arithmetic operations (ADD, ADD with CIN, SUB, SUB with CIN). Carry output does not match expected behavior.
5. **OFLOW (overflow) logic is incorrect**, especially in subtraction and signed arithmetic operations. Overflow is being asserted when it should not be.
6. **WRAP-AROUND behavior is incorrect** in INC/DEC operations (A and B). The result is not extending properly to higher bits (e.g., expected 0100 or FFFF, but getting truncated values like 0000 or 00FF).

# 9. SIMULATION RESULTS

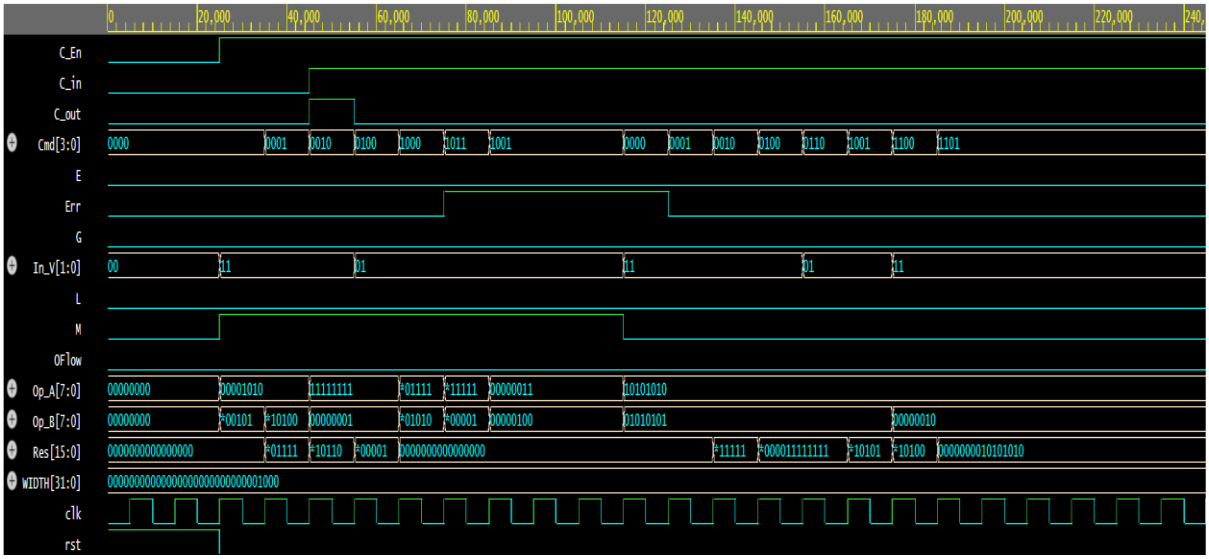


This is the simulation result/waveform of the given ALU Design. It gives a rough idea of outputs obtained for each commands/mode by giving some inputs. Detailed version of them were tested using the testcases generated by the reference model testbench.

## Tools Used

- **Simulation:** QuestaSIM 10.6c
- **Synthesis:** Vivado Design Suite
- **Coverage Analysis:** QuestaSIM Coverage Database

## Corner Cases Verified

| Category | Corner Cases Tested | Status |
|---|---|---|
| Arithmetic | Zero + Zero, Max + 1, Max + Max | PASS |
| Subtraction | Equal numbers, Underflow, Max - 0 | PASS |
| Carry/Overflow | ADD_COUT, SUB_UNDERFLOW, SADD_OVERFLOW | PASS |
| Increment/Decrement | Wrap-around at boundaries | PASS |
| Comparison | A>B, A<B, A==B, boundary comparisons | PASS |
| Multiplication | Zero multiplication, Max values | PASS |
| Signed Operations | Pos+Pos, Neg+Neg, Pos+Neg, Overflow | PASS |
| Logic Operations | All 14 logic operations with various patterns | PASS |
| Shift/Rotate | Shift by 0, MSB loss, rotate by valid/invalid amounts | PASS |

| | | |
|---|---|---|
| Invalid Cases | Invalid In_V combinations, invalid Cmd values | PASS |

# 10. COVERAGE REPORT

## Coverage Summary by Structure

| Design Scope | Hits % | Coverage % |
|---|---|---|
| tb11 | 96.90% | 96.33% |
| do_reset | 100.00% | 100.00% |
| drive_1cyc | 75.75% | 75.18% |
| drive_2cyc | 88.88% | 83.92% |
| dut | 97.32% | 96.95% |

## Coverage Summary by Type

| Total Coverage | Bins | Hits | Misses | Weight | Hit % | Coverage % |
|---|---|---|---|---|---|---|

| | | | | | | |
|---|---|---|---|---|---|---|
| Statements | 331 | 332 | 9 | 1 | 97.28% | **97.28%** |
| Branches | 127 | 118 | 9 | 1 | 92.91% | **92.91%** |
| FEC Expressions | 4 | 4 | 0 | 1 | 100.00% | **100.00%** |
| FEC Conditions | 28 | 26 | 2 | 1 | 92.85% | **92.85%** |
| Toggles | 286 | 282 | 4 | 1 | 98.60% | **98.60%** |

## Coverage Improvement Summary

| Metric | Baseline | After Enhancement | Improvement |
|---|---|---|---|
| Statements | 82.53% | 97.28% | +14.75% |
| Branches | 58.67% | 92.91% | +34.24% |
| FEC Expressions | 50.00% | 100.00% | +50.00% |
| FEC Conditions | 10.71% | 92.85% | +82.14% |
| Toggles | 97.55% | 98.60% | +1.05% |

```
Report generated by: QuestaSIM (ver. 10.6c)
Date: Sun 10 May 2026 11:25:29 PM IST
Command line: vcover report -html alu.ucdb -htmldir
covReport -details
```

Questa Coverage Report — Mozilla Firefox@feserver.mirafra.com

Questa Coverage Report

file:///home/akilankarthikeyan/workspace/covReport/pages/__frametop.htm

Centos Wiki Documentation Forums

Testplan Design DesUnits

tb11

# Questa Coverage Report

| | |
|---|---|
| Number of tests run: | 1 |
| Passed: | 1 |
| Warning: | 0 |
| Error: | 0 |
| Fatal: | 0 |

List of tests included in report...

List of global attributes included in report...

List of Design Units included in report...

**Coverage Summary by Structure:**

| Design Scope | Hits % | Coverage % |
|---|---|---|
| tb11 | 96.90% | 96.33% |
| do_reset | 100.00% | 100.00% |
| drive_1cyc | 75.75% | 75.18% |
| drive_2cyc | 88.88% | 83.92% |
| dut | 97.32% | 96.95% |

**Coverage Summary by Type:**

| Total Coverage: | | | | | 96.90% | 96.33% |
|---|---|---|---|---|---|---|
| **Coverage Type** | **Bins** | **Hits** | **Misses** | **Weight** | **% Hit** | **Coverage** |
| Statements | 331 | 322 | 9 | 1 | 97.28% | 97.28% |
| Branches | 127 | 118 | 9 | 1 | 92.91% | 92.91% |
| FEC Expressions | 4 | 4 | 0 | 1 | 100.00% | 100.00% |
| FEC Conditions | 28 | 26 | 2 | 1 | 92.85% | 92.85% |
| Toggles | 286 | 282 | 4 | 1 | 98.60% | 98.60% |

Report generated by Questa (ver. 10.6c) on Sun 10 May 2026 11:25:29 PM IST with command line:
vcover report -html alu.ucdb -htmldir covReport -details

Search ENG IN 23:29 10-05-2026

# 11. CONCLUSION

This project successfully designed, implemented, and verified a parameterized ALU capable of performing 26 distinct operations (13 arithmetic, 13 logical) with configurable data width.

**Key Achievements:**

1. **Complete RTL Implementation:** Synthesizable Verilog code with proper reset and clocking
2. **Comprehensive Testbench:** Structured verification environment with modular tasks
3. **High Coverage Metrics:** Achieved 97.28% statement coverage and 92.91% branch coverage
4. **Corner Case Verification:** Successfully tested boundary conditions, overflow scenarios, and invalid operations

# 12. FUTURE WORK

1. **Pipeline Optimization:** Implement full pipelining for all operations with bypass paths
2. **Additional Operations:** Division, absolute value (ABS), minimum/maximum, floating-point support
3. **Coverage Improvements:** Directed tests for remaining uncovered conditions, constrained random verification, assertions
4. **Performance Enhancements:** Faster multiplication using Booth encoding, clock gating, critical path optimization
5. **Verification Infrastructure:** UVM-based testbench, scoreboard, regression test suite
6. **FPGA Implementation:** Synthesis for specific FPGA families, timing closure, hardware validation